

# An Effective Model of Bucket- Brigade Device-Based Audio Circuits


Colin Raffel  
CCRMA DSP Seminar  
May 7th, 2010

# Contents

- History and Topology
- Circuit examples
- Anti-aliasing and reconstruction filters
- Compression and expansion
- Bucket brigade device effects
- Modeling
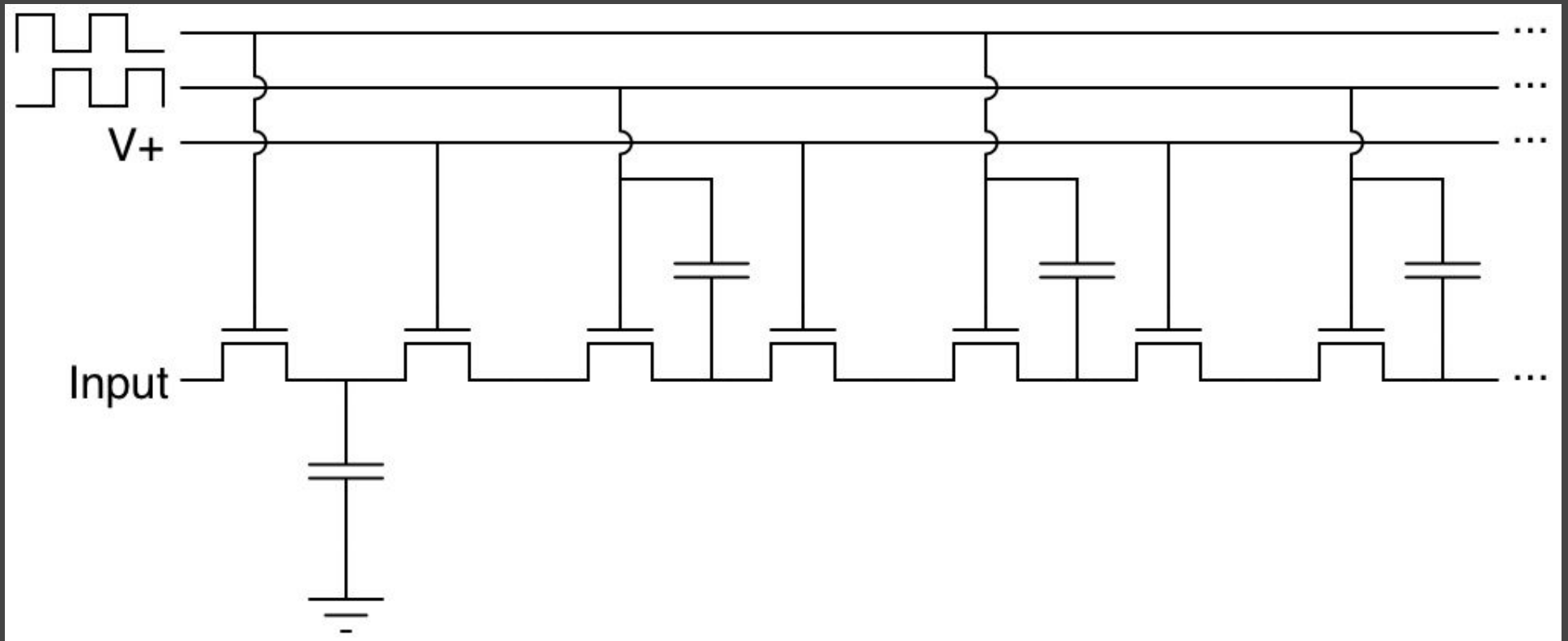
# Topology


- Invented by Sangster at Philips, 1968
- Sampled signal passed through capacitors at clock rate (bucket brigade analogy)
- Early implementations proved to be overly inefficient
- Improved by Sangster and Reticon Corporation in the 1970s - each capacitor is separated by a DC biased gate
- Architecture widely used (by Panasonic, Reticon, and Philips) until digital delays became cheaper




*Antiphase-clock bucket brigade circuit found in most BBD integrated circuits.*
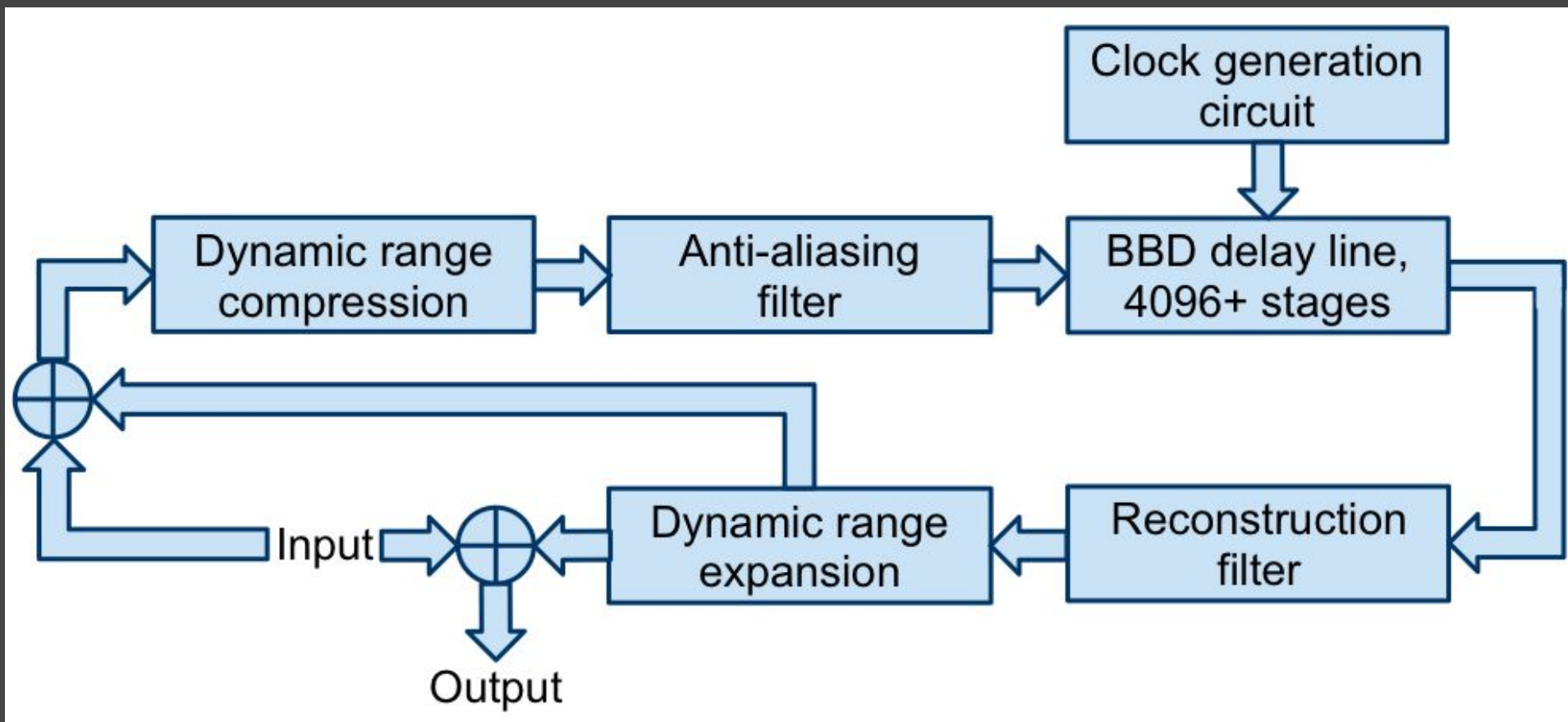
# Circuit Examples

- Echo circuits
  - Many-thousand-stage delay line
  - Highly variable clock frequency
  - Anti-aliasing and reconstruction filters
  - Compression, expansion
  - Feedback (repeating echo)
- Chorus, Vibrato, Flanger
  - ~1,000 stages
  - LFO varies clock frequency
  - Anti-aliasing and reconstruction filters
  - Feedback in some cases



Commonly implemented BBD echo block diagram

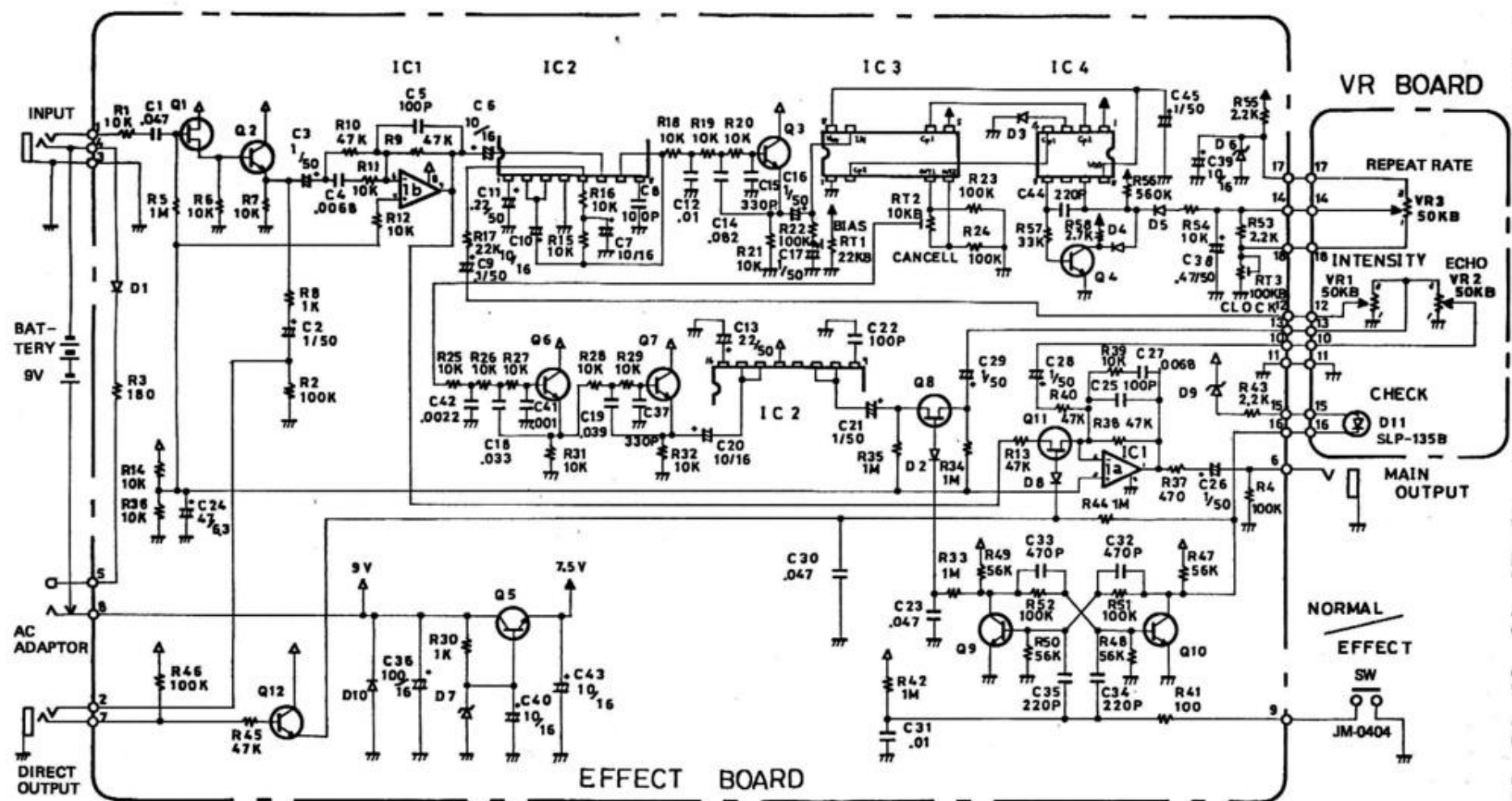


IC1 : NJM4568DD  
IC2 :  $\mu$ PC1571C  
IC3 : MN3205  
IC4 : MN3102

O4,5,9,10,12 : 2SC1685-R  
or 2SC945-P  
Q2,3,6,7 : 2SC732TM-GR  
Q1,8,11 : 2SK30ATM-Y

D1-5,8 : 1S2473  
D6 : RD5.6JB2  
D7 : RD8.2EB3  
D9 : RD5.6EB3  
D10 : S5500G


BOSS DM-3 circuit diagram



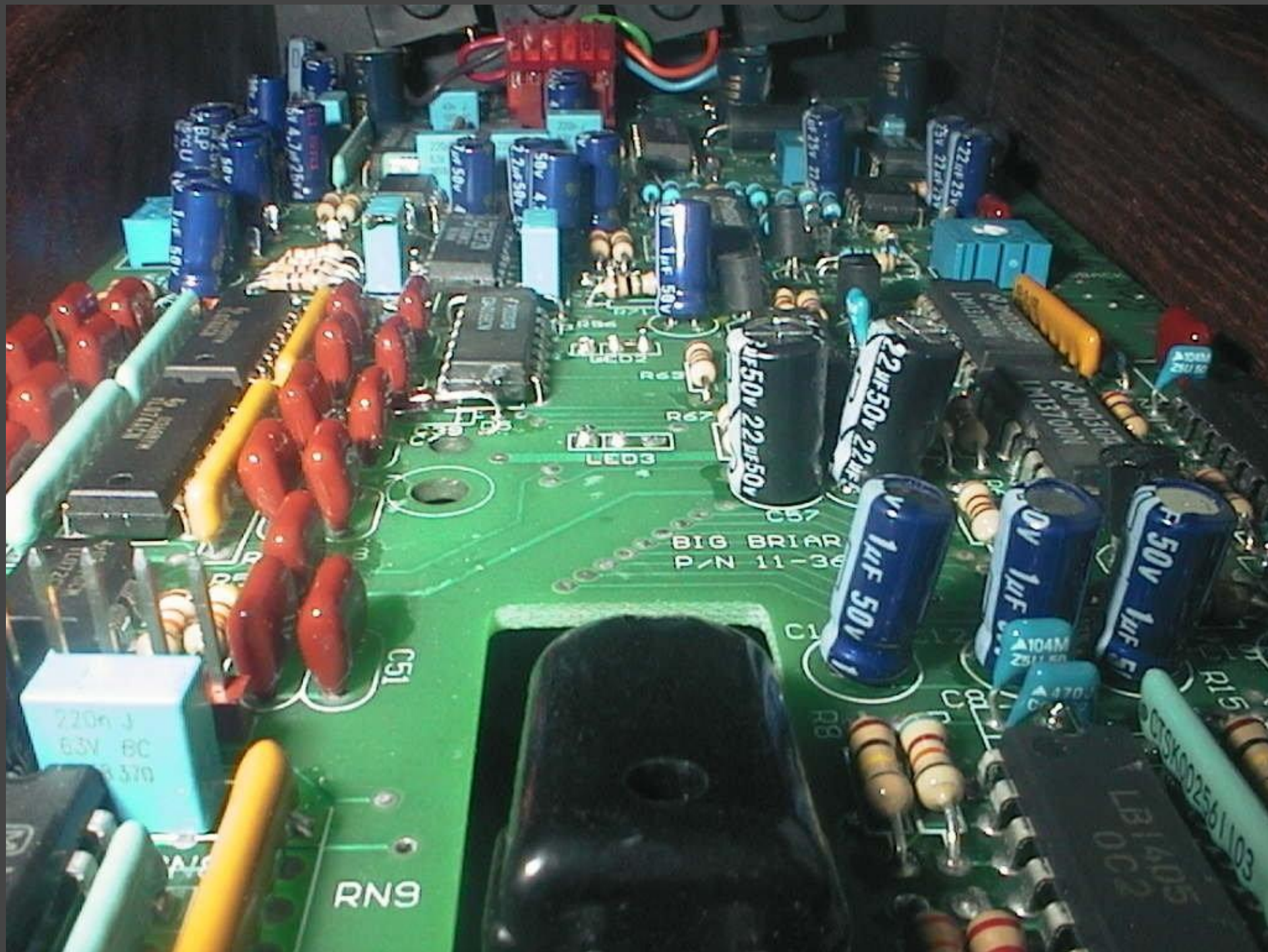


*Moog MF-104Z Delay*



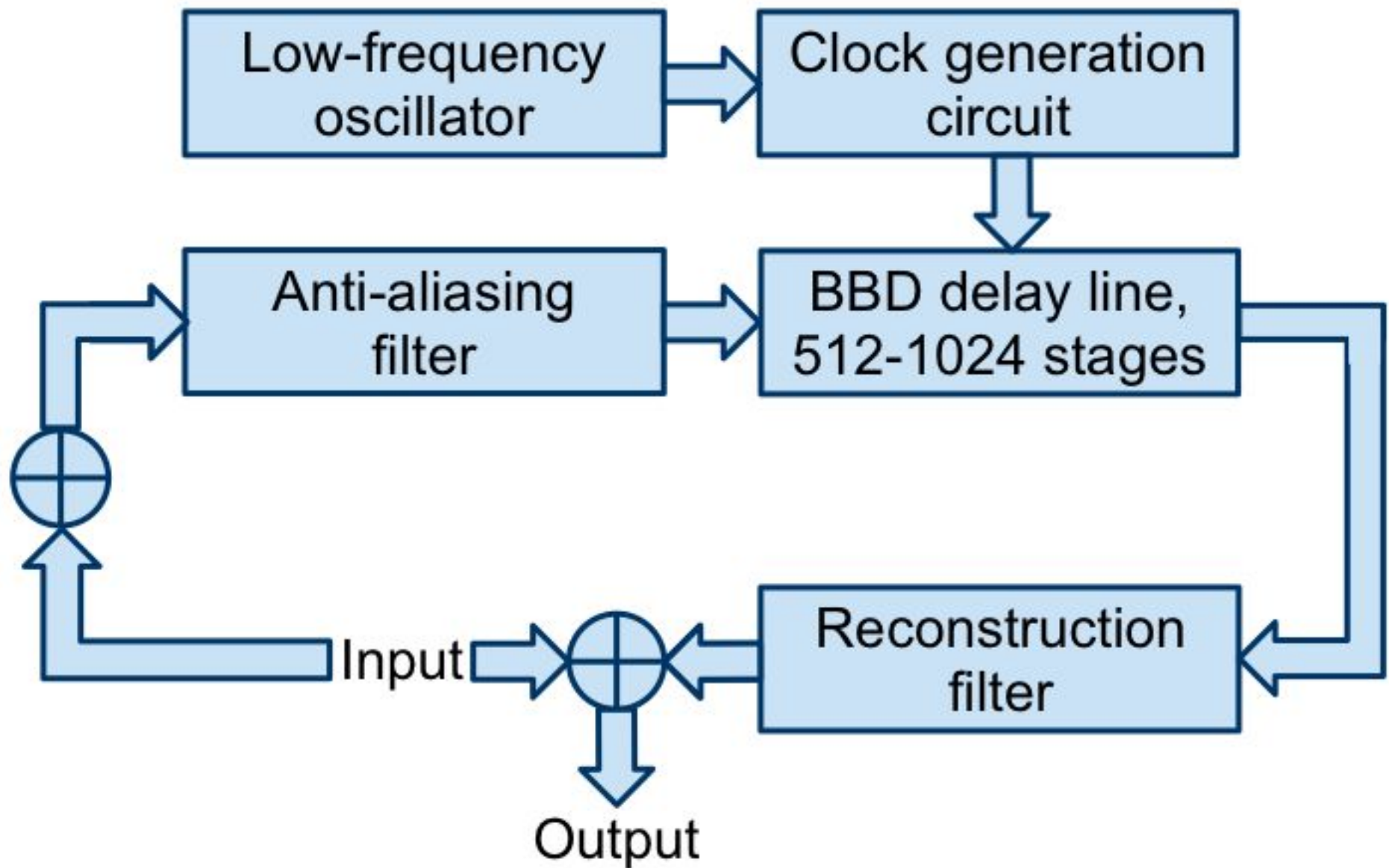

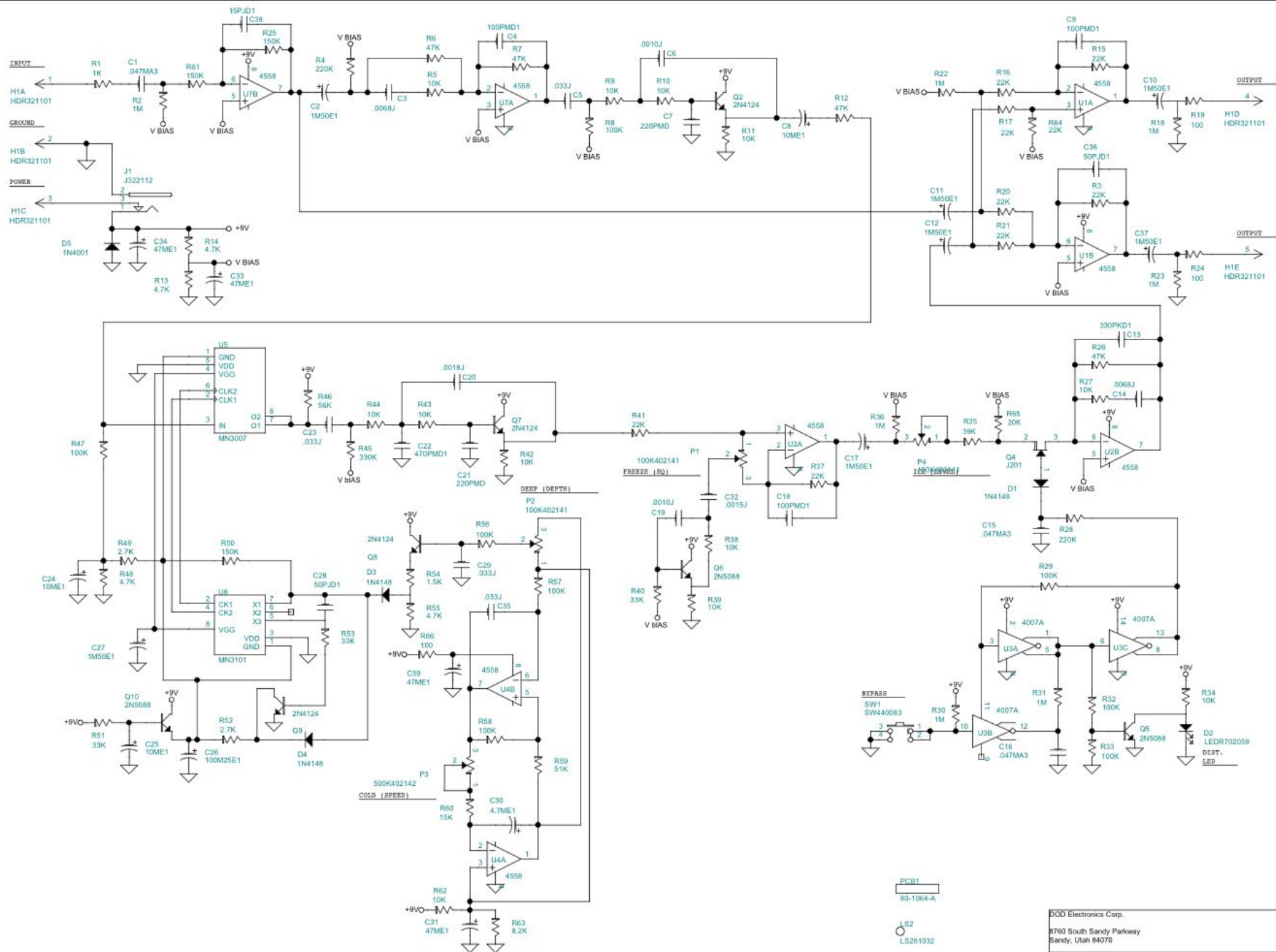*Commonly implemented chorus block diagram*





DOD Electronics Corp.		
8760 South Sandy Parkway Sandy, Utah 84070		
File		
FX64 ICE BOX 80-1064		
Size		
B	Document Number	Rev
	050064A2.001	A2
Date: Thursday, December 16, 1999 Sheet 1 of 1		

*DOD Icebox Chorus circuit diagram*

# Filtering Requirements

$$\text{Delay Time (s)} = \frac{N}{2f_{cp}}$$


- Echo Circuits
  - Common implementation: 300 ms delay time with 4096 stages
  - ~7 kHz clock frequency
  - Sometimes as low as ~4 kHz!
- Chorus Circuits
  - 10 ms delay with 1024 stages
  - 51.2 kHz clock frequency
  - Sometimes lower
- Anti-aliasing and reconstruction filters needed

# Filter Implementation

- Sallen-Key lowpass filters
  - Transistor-based common
  - Op-amp-based less common


$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{\frac{1}{R^2 C_1 C_2}}{s^2 + \frac{2s}{RC_1} + \frac{1}{R^2 C_1 C_2}}$$

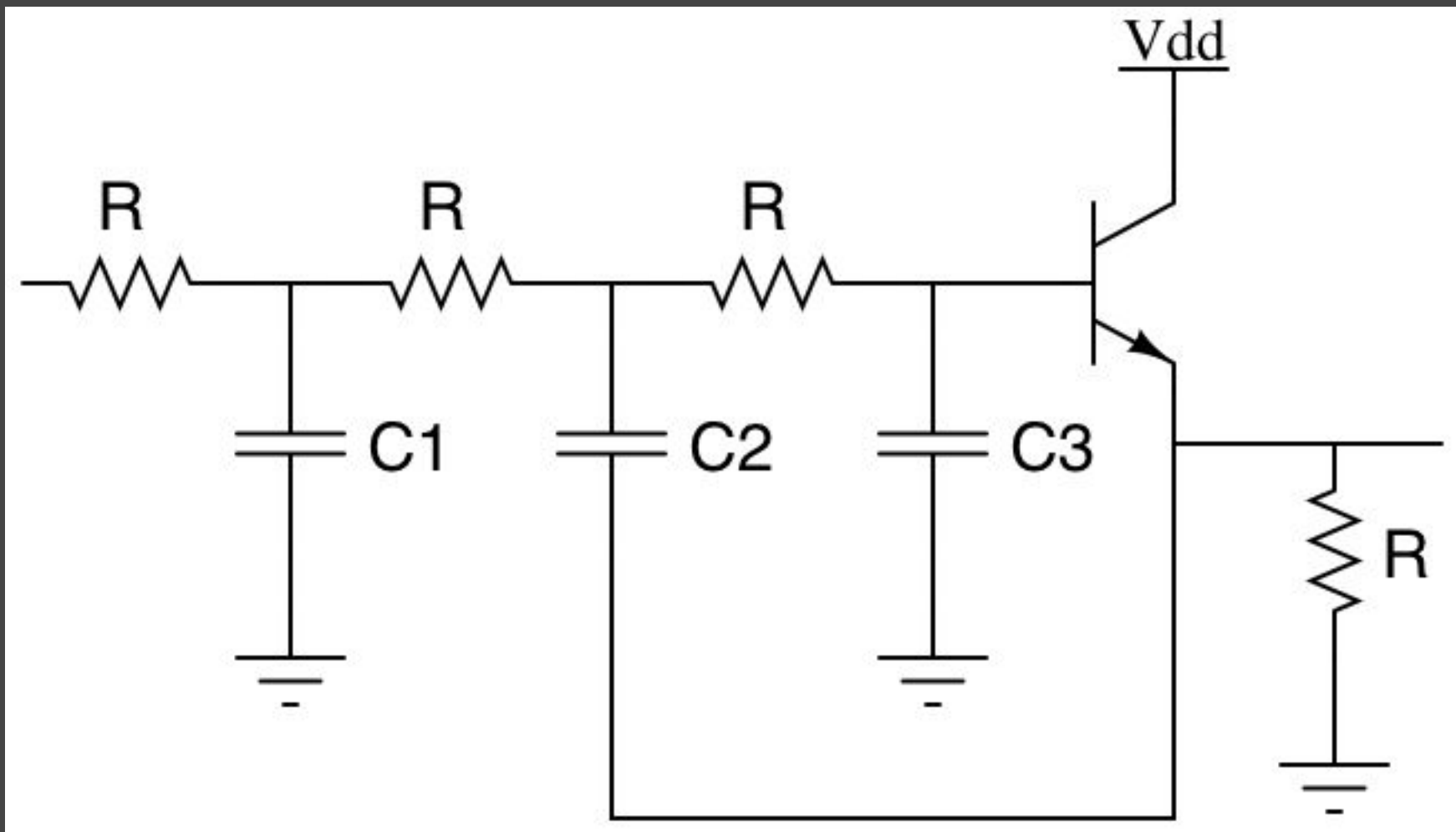- Cutoff frequency typically chosen to be 1/3 to 1/2 of the BBD clock
- In echo circuits, third-order anti-aliasing, and series third- and second-order reconstruction
- In chorus, flanger, and vibrato, typically lower total order
- Switched-capacitor filters rare, but smart




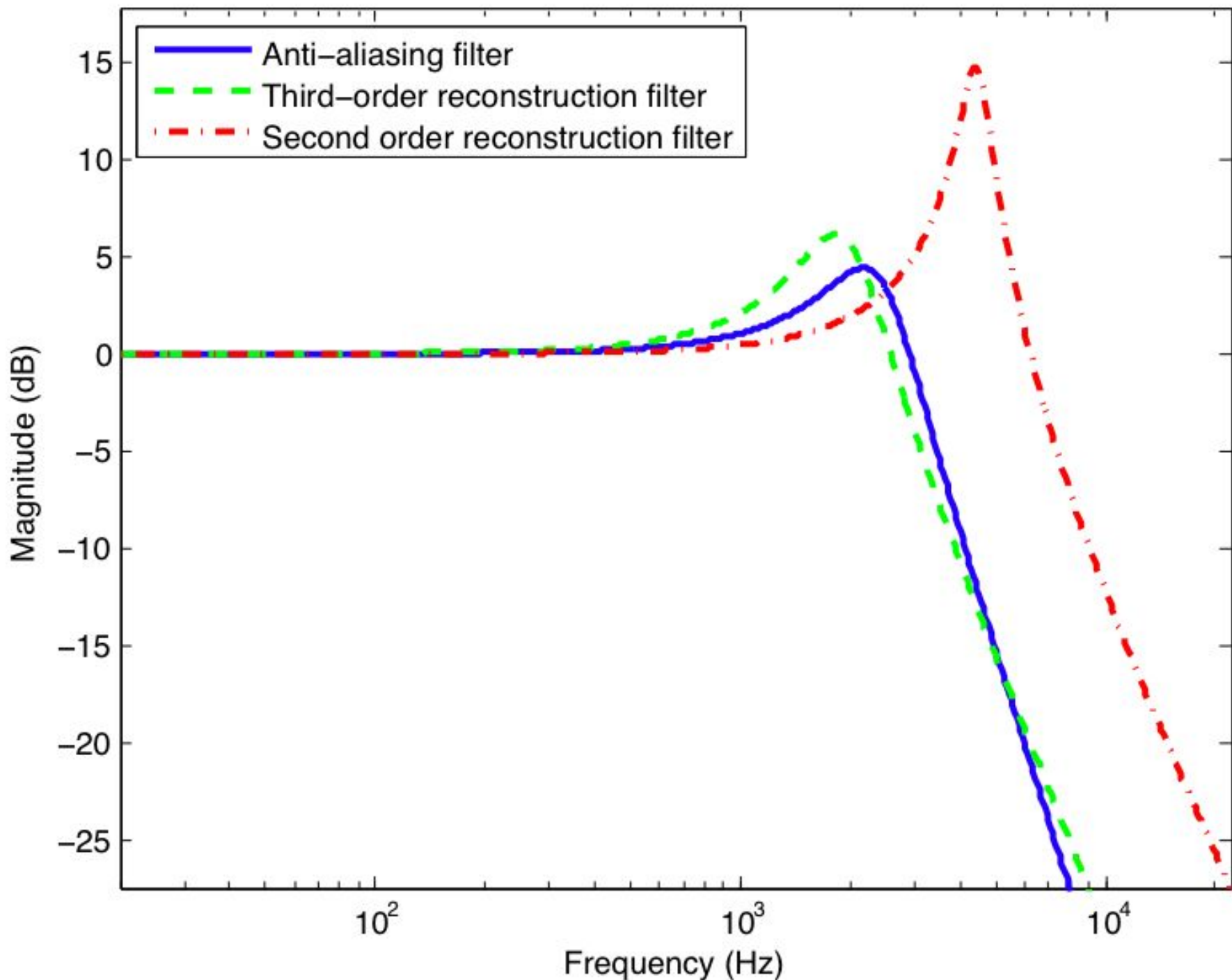*Third-order, transistor-based Sallen-Key low-pass filter*






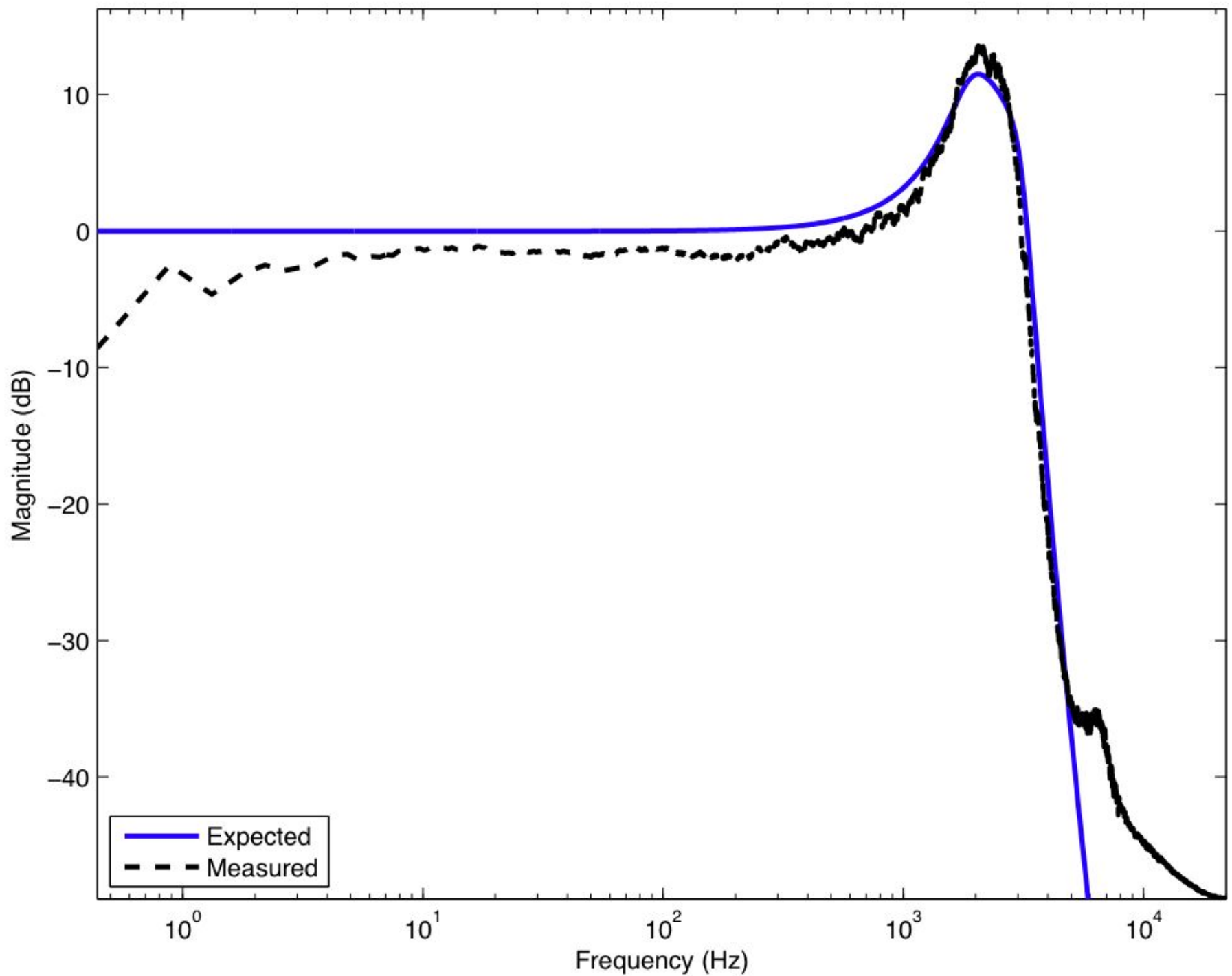
*Typical magnitude responses of anti-aliasing filter and reconstruction filters*



*Measured and calculated combined magnitude response*
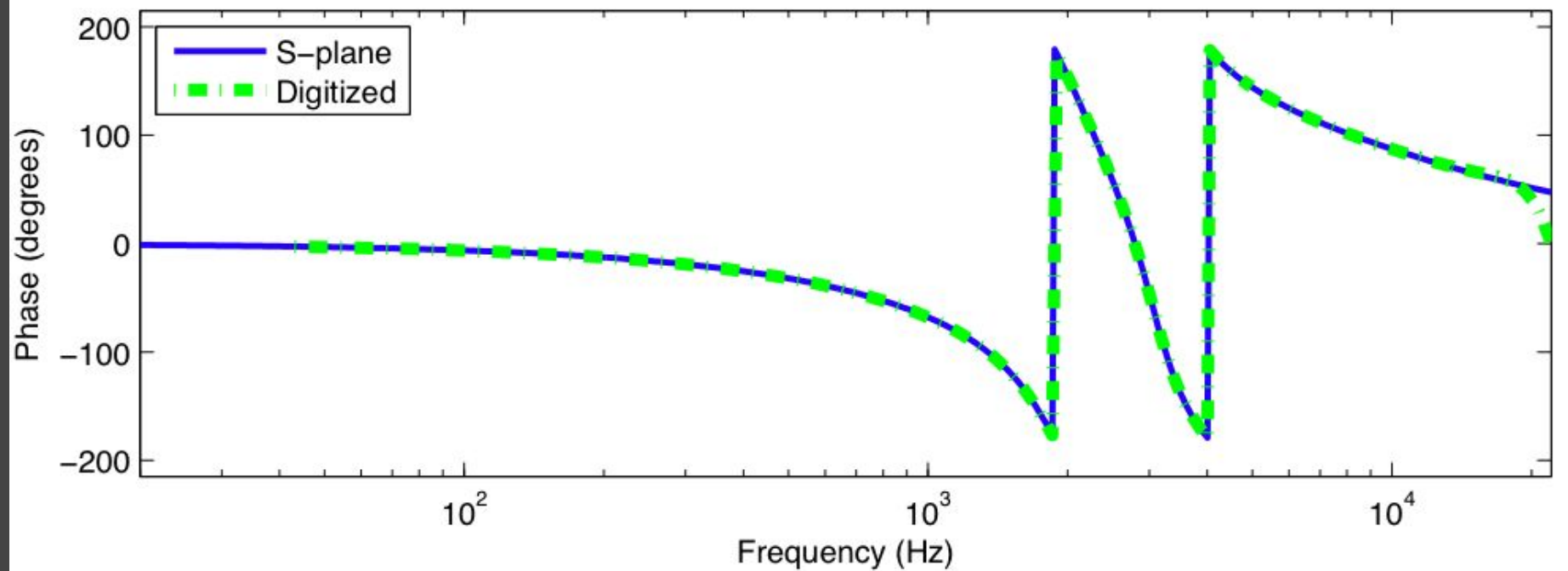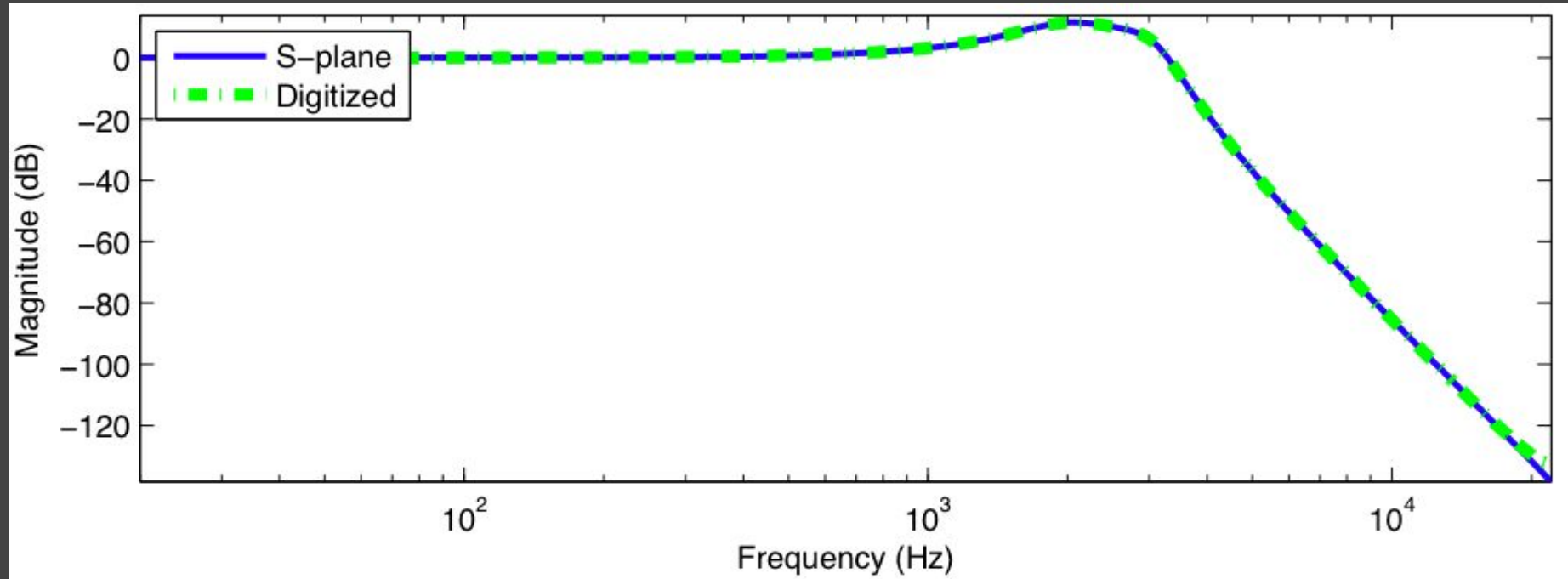
# Modeling BBD Filters


- First, obtain a frequency response based on circuit values and Sallen-Key filter transfer functions (or direct measurements)
- Then, digitize using any of a number of filter design methods (for example, `invfreqz`)
- Highly accurate filters are possible at relatively low-orders
  - Third order ~5-7
  - Second order ~2
  - Total ~9
- Filter representation is often the most perceptually relevant part of the model



*Digitized combined filter response, ninth-order*
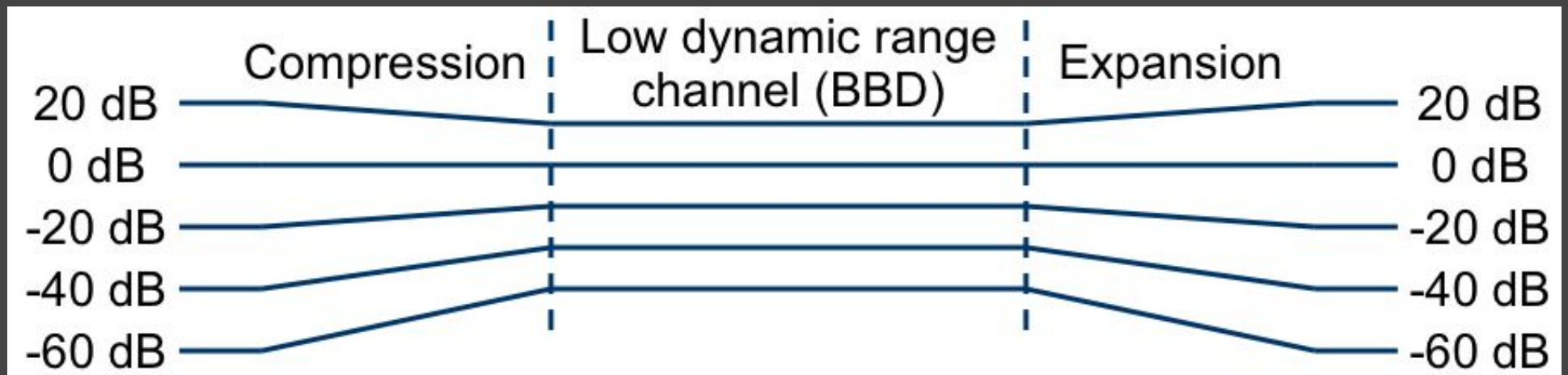
# Companing

- BBDs have a low dynamic range
  - ~60 dB SNR common
  - THD increases dramatically when amplitude is over about 10% of the supply voltage
  - Effects are worse as the number of stages increases
- Companing
  - Compression preceding the BBD
  - Expansion following the BBD
  - Results in a low dynamic range in the BBD "channel"
  - Normally only found in echo circuits



*Effect of companding on the dynamic range of a signal*



# 570- and 571-series

- The majority of BBD systems which include a compander use the 570- or 571-series compander
- Pair of variable gain amplifiers and level detectors
- Gain is internally set to have a compression or expansion ratio of 2
- Level detector controlled by external capacitor
  - Internally, the signal is rectified and sent through a RC filter
  - Resistor is internally set to 10kOhm
  - Capacitor value chosen to minimize ripple

$$\tau = 10000C_{rect}$$

# Modeling BBD Compansion

- Use the average signal level to determine the gain of the system
  - Expander (feedforward)

$$f(x) = \text{avg}(|x|)x$$

- Compressor (feedback)

$$f(x) = \frac{x}{\text{avg}(|f(x)|)}$$

- Averaging circuitry can be modeled by a one-pole digital filter
  - Input should be rectified
  - Model easily calculated based on external capacitor value

$$y(n) = x(n) \frac{T}{RC + T} + y(n-1) \frac{RC}{RC + T}$$

# BBD Aliasing

- Discrete-time sampling produces large amounts of aliasing distortion
- This effect is ideally (and mostly) removed by anti-aliasing and reconstruction filters
- Modeling approaches
  - Can be ignored, but an interpolating delay line should be used
  - Downsampling/upsampling more realistic
  - Delay line of fixed length with "virtual" BBD clock source is most accurate and gives pitch shifting when changing the delay time for free

# Insertion gain

- BBDs have a "frequency-dependent" insertion gain (filtering)
- Can be thought of as not being able to transfer charge at speeds near the Nyquist limit
- Varies with clock frequency and number of stages
- Typically between 0 to 2 dB for lower frequencies, down to -4 to -6 dB near the Nyquist limit
- Much less dramatic than anti-aliasing and reconstruction filters
- Digital filters based on measured response could model this effect


# BBD Noise

- BBDs introduce noise, SNR typically ~60 dB
- Result of imperfect transactions between BBD stages
- Varies slightly with number of stages and clock frequency
- Can be reduced, but not removed, by compansion
- Inclusion in the model depends on application
  - Can be omitted for an intentionally clean digital system
  - Must be included to realize the "self-oscillation" effect common to BBD-based echos

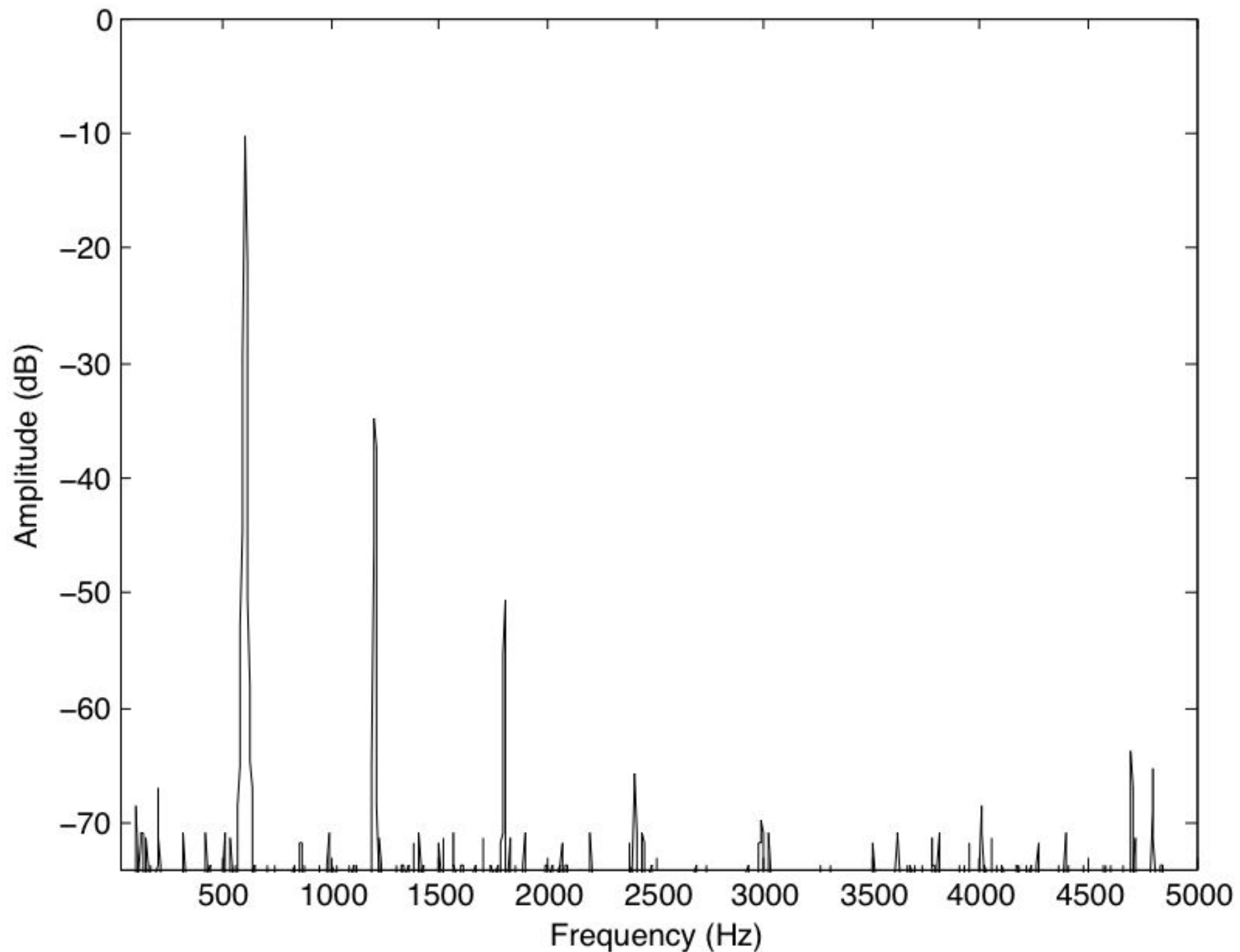
# Nonlinearities

- THD typically rated and measured to be about 1% per 1024 BBD stages
  - Hardly apparent for choruses, vibratos, and flangers
  - More apparent in echos, where the signal is recirculated
- Minimized by biasing input signal
- Does not vary dramatically with signal level (separate from BBD clipping)
- Aliasing distortion makes measurement difficult





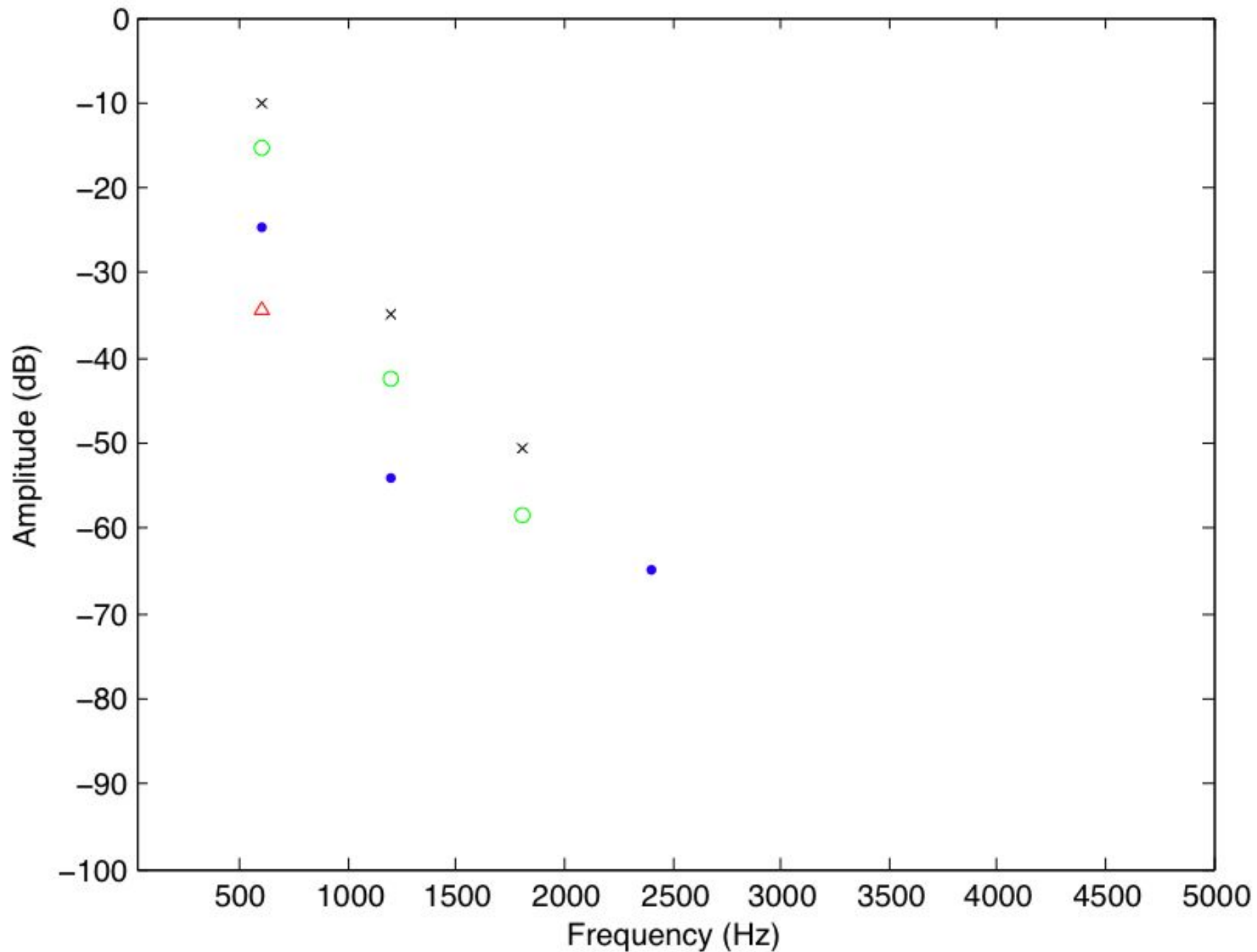*Measured magnitude spectrum for pure sine tone input*




*Peaks in magnitude spectrum for pure sine wave inputs at various levels*

# Nonlinearity Modeling

- Modeling is difficult because it is not a "clipping" nonlinearity
- Polynomial nonlinearity provides a good estimate

$$f(x) = \begin{cases} 1 - a - b & \text{for } x > 1 \\ x - ax^2 - bx^3 + a & \text{for } -1 < x < 1 \\ -1 - a + b & \text{for } x < -1 \end{cases}$$

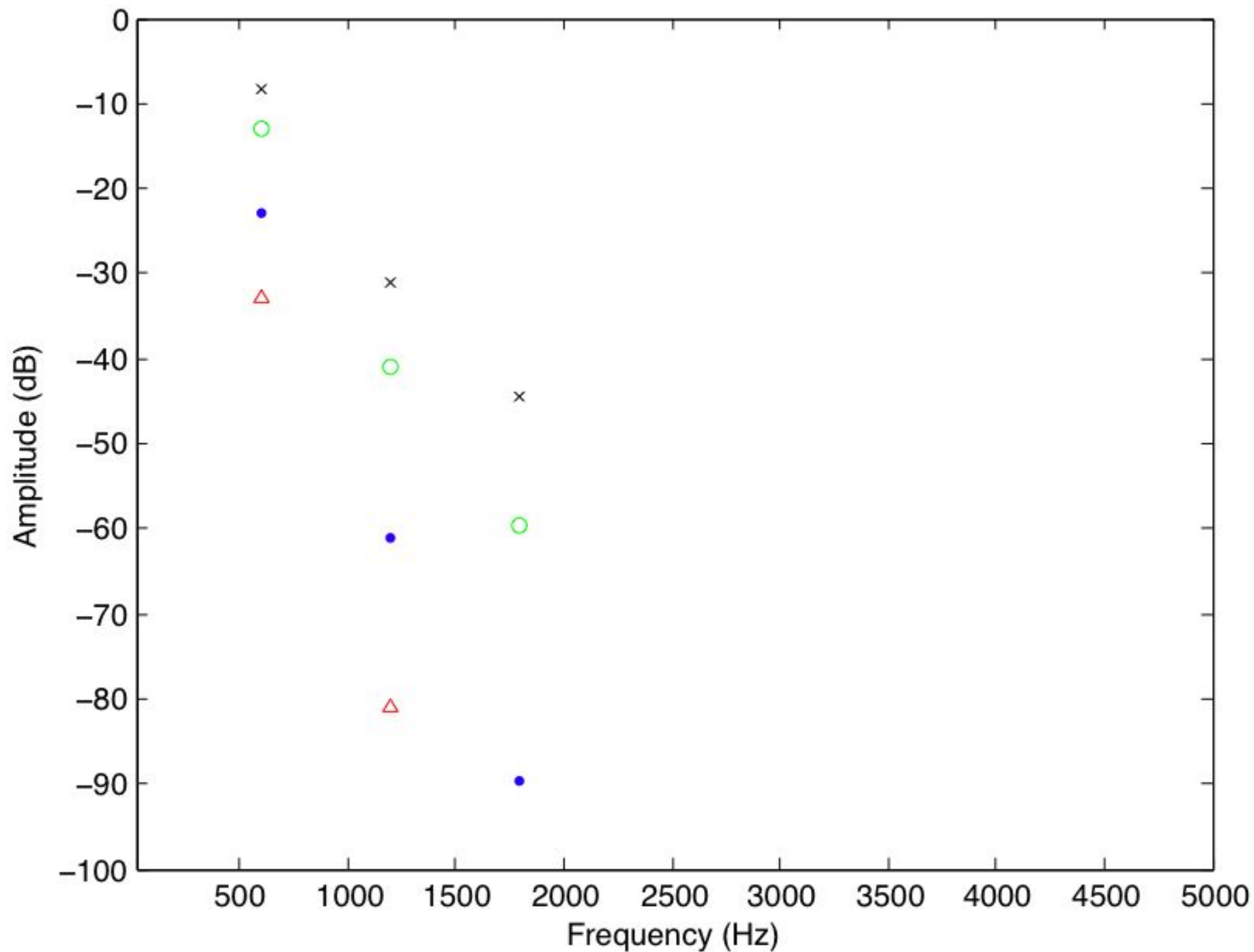- Parameters can be chosen to match one particular sine wave input level
- A more accurate implementation could vary parameters based on the average signal level
- Anti-aliasing filter in BBD system conveniently reduces digital nonlinearity aliasing problems



*Harmonic distortion resulting from nonlinearity model*

# Model Example

- Models a 4096-stage BBD echo circuit
- Includes compansion, filtering, "virtual clock", noise, and nonlinearities
- Practical difficulties
  - Feedback compressor creates a delay-free loop
  - "Virtual clock" implementation results in excessive aliasing distortion due to "clock jitter"
  - Compander estimate not exact
  - Component values also vary filter response

# Acknowledgements

- Adam Sheppard and Travis Skare for lending BBD-based circuits to measure
- David Yeh for help identifying filter topologies
- Jonathan Abel for suggestions on where to look for BBD imperfections
- Julius Smith for practical advice and giving me the opportunity to study this!



# Further Reading

- "Practical Modeling of Bucket Brigade Device Circuits" paper
- References therein
- Datasheets and circuit diagrams
  - <http://www.sdiy.org/BBDHell/BBD-Manual.pdf>
  - <http://experimentalistsanonymous.com/diy/>